

Depletion-Mode Power MOSFETs and Applications

Abdus Sattar, IXYS Corporation

Applications like constant current sources, solid-state relays, telecom switches and high voltage DC lines in power systems require N-channel Depletion-mode power MOSFET that operates as a normally “on” switch when the gate-to-source voltage is zero ($V_{GS}=0V$). This paper will describe IXYS latest N-Channel Depletion power MOSFETs and their application advantages to help designers to select these devices in many industrial applications.

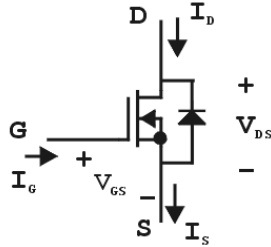


Figure 1: An N-channel Depletion-mode power MOSFET

A circuit symbol for N-channel Depletion-mode power MOSFET is given in Figure 1. The terminals are labeled as G (gate), S (source) and D (drain). IXYS Depletion-mode power MOSFETs are built with structure called vertical double-diffused MOSFET or DMOSFET and have better performance characteristics compare to other depletion-mode power MOSFETs on the market such as high V_{DS} , high current and high forward-biased safe operating area (FBSOA).

Figure 2 shows a typical drain current (I_D) versus the drain-to-source voltage (V_{DS}) characteristics called the output characteristic. It's a similar plot to that of an N-channel Enhancement-mode power MOSFET except that it has current lines at V_{GS} of -2V, -1V, and 0V.

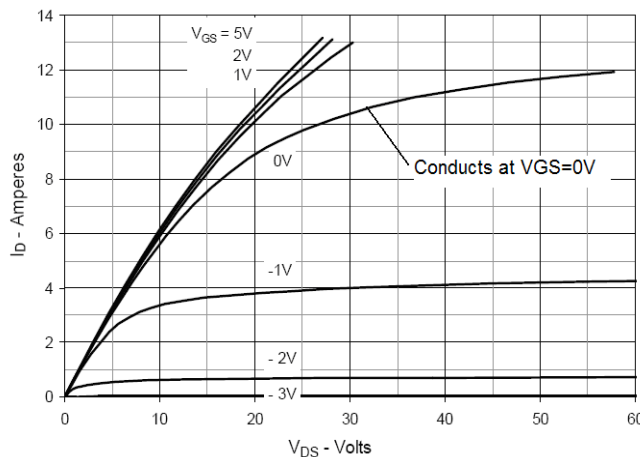


Figure 2: Output characteristics of N-channel Depletion-mode power MOSFET

The on-state drain current, $I_{D(on)}$, a parameter defined in the datasheet, is the current that flows between the drain and the source at a particular drain-to-source voltage (V_{DS}), when the gate-to-source voltage (V_{GS}) is zero (or short-circuited). By applying positive gate-to-source (V_{GS}) voltage, the device increases the current conduction level. On the other hand, the negative gate-to-source (V_{GS}) voltage reduces the drain current. As shown in Figure 2, the device stops conducting the drain current at $V_{GS} = -3V$. This $-3V$ is called the gate-to-source cutoff voltage or threshold voltage ($V_{GS(off)}$) of the device. In order to ensure proper turn on, the applied gate-to-source (V_{GS}) voltage should be close to $0V$ and to proper turn off, a more negative V_{GS} voltage than the cutoff voltage ($V_{GS(off)}$) should be applied. Theoretically, the on-state drain current, $I_{D(on)}$, can be defined as,

$$I_D = I_{D(on)} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 \quad (1)$$

Note that the equation (1) is a theoretical formula, which in most cases would not estimate an accurate value of the drain current. $V_{GS(off)}$ has a range of $-4V$ to $-2V$ and $I_{D(on)}$ depends both on $V_{GS(off)}$ and the temperature.

A list of IXYS N-channel discrete Depletion-mode power MOSFETs is given in Table 1. The table shows the device's four main parameters: the drain-to-source breakdown voltage (V_{DSX}), the on-state drain current ($I_{D(on)}$), the on-state resistance ($R_{DS(on)}$) and the gate-to-source cutoff voltage ($-V_{GS(off)}$) along with standard discrete package options such TO-263 (D2-PAC), TO-220, TO-247, TO-252 (D-PAC) and TO-251 (I-PAC).

Table 1: IXYS N-channel Depletion-mode power MOSFETs

Part No	V_{DSX} (V)	$I_{D(on)}$ (A)	$R_{DS(on)}$ (Ohm)	$V_{GS(off)}$ (V)	Package Type
IXTH16N10D2	100	16	0.064	-4.0	TO-247
IXTT16N10D2	100	16	0.064	-4.0	TO-268
IXTH16N20D2	200	16	0.073	-4.0	TO-247
IXTT16N20D2	200	16	0.073	-4.0	TO-268
IXTA6N50D2	500	6	0.5	-4.0	TO-263
IXTH6N50D2	500	6	0.5	-4.0	TO-247
IXTA6N50D2	500	6	0.5	-4.0	TO-220
IXTT6N50D2	500	6	0.5	-4.0	TO-268
IXTA3N50D2	500	3	1.5	-4.0	TO-263
IXTA3N50D2	500	3	1.5	-4.0	TO-220
IXTH3N50D2	500	3	1.5	-4.0	TO-247
IXTA1R6N50D2	500	1.6	2.3	-4.0	TO-263
IXTA1R6N50D2	500	1.6	2.3	-4.0	TO-220
IXTY1R6N50D2	500	1.6	2.3	-4.0	TO-252
IXTA08N50D2	500	0.8	4.6	-4.0	TO-263
IXTA08N50D2	500	0.8	4.6	-4.0	TO-220
IXTY08N50D2	500	0.8	4.6	-4.0	TO-252
IXTA02N100D2	1000	0.2	75	-5.0	TO-263

IOTP02N100D2	1000	0.2	75	-5.0	TO-220
IXTU02N100D2	1000	0.2	75	-5.0	TO-251
IXTY02N100D2	1000	0.2	75	-5.0	TO-252
IXTA6N100D2	1000	6	2.2	-4.5	TO-263
IXTH6N100D2	1000	6	2.2	-4.5	TO-247
IOTP6N100D2	1000	6	2.2	-4.5	TO-220
IXTA3N100D2	1000	3	5.5	-4.5	TO-263
IOTP3N100D2	1000	3	5.5	-4.5	TO-220
IXTA1R6N100D2	1000	1.6	10	-4.5	TO-263
IOTP1R6N100D2	1000	1.6	10	-4.5	TO-220
IXTY1R6N100D2	1000	1.6	10	-4.5	TO-252
IXTA08N100D2	1000	0.8	21	-4.0	TO-263
IOTP08N100D2	1000	0.8	21	-4.0	TO-220
IXTY08N100D2	1000	0.8	21	-4.0	TO-252

Selecting a Depletion-mode Power MOSFET

The depletion-mode power MOSFET will function in those applications requiring a normally on-switch. The main selection criteria for a Depletion-mode MOSFET based on the application are as follows:

1. Pick the package first and look at the products available that meet the application requirements.
2. Select the breakdown voltage meeting the margin for reliable operation
~ BV_{DSX} , the drain-to-source breakdown voltage

The application voltage must be lower than the drain-to-source breakdown voltage of the device. BV_{DSX} needs to be selected to accommodate the voltage swing between the bus positive and the bus negative as well as any voltage peaks caused by voltage ringing due to transients.

3. Identify the current requirement and pick a package capable of handling that current
~ $I_{D(on)}$, the on-state drain current

The application current must be lower than the on-state drain current of the device.

It is the maximum current that can flow between the drain and source, which occurs at a particular drain-to-source voltage (V_{DS}) and when the gate-to-source voltage (V_{GS}) is zero.

4. $V_{GS(off)}$, the gate-to-source cutoff voltage

N-Channel Depletion-mode MOSFET has negative channel cutoff voltage, which is designated as $V_{GS(off)}$. A designer has to know well the magnitude of the negative cutoff voltage (or threshold voltage). A negative gate-to-source voltage (V_{GS}) will reduce the drain current until the device's cutoff voltage level is reached and the conduction ceases.

Applications

Figure 3 shows a very precise current source to the load RL1. TL431 is a programmable voltage reference IC. The feedback voltage from the sense resistor RS1 is controlled to be 2.5V. It will operate as a current source at any current level below the device's rated current rating, $I_{d(on)}$.

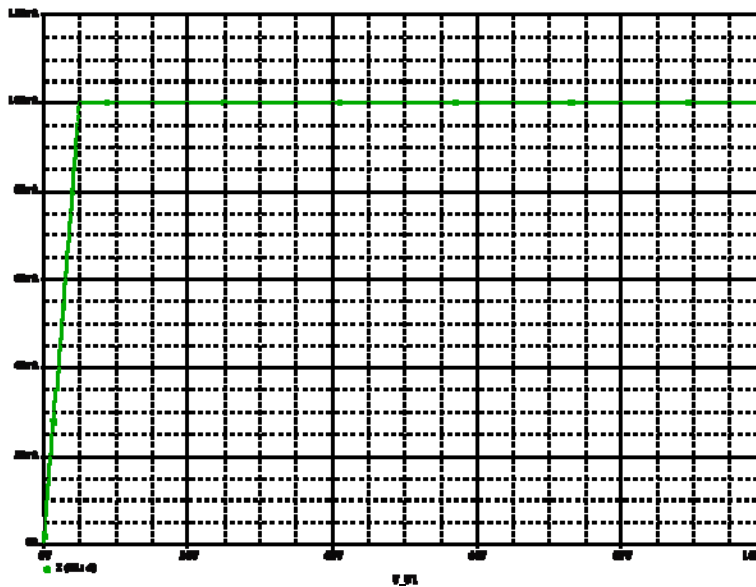
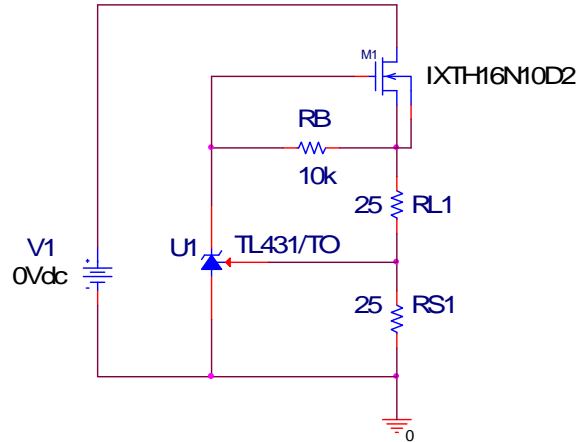


Figure 3: Depletion-mode MOSFET current source and the current waveform

The theoretical sense resistor value is given by

$$R_S = \frac{V_{GS(off)}}{I_D} \left[1 - \sqrt{\frac{I_D}{I_{D(on)}}} \right] \quad (2)$$

Note that the equation (2) is a theoretical formula which mostly would not estimate the practical values of R_s . In most cases, it's convenient to use a potentiometer to set the desired current level.

Design example,
 IXTA1R6N50D2 with $I_{D(on)}$ of 1.6A, a $V_{GS(off)}$ of -4.0V, V_{DSX} of 500V.
 Design a current source of 100mA. The required value of R_s would be equal ~ 40 ohms.
 Choose a wide range of +V, for example from 20V-400V.

Figure 4 shows another constant current source with Depletion-mode MOSFET, Q1 and the gate-to-source Zener diode DZ1. The required V_{GS1} will determine the necessary resistor value for R1 using the same formula (2). This design may useful in higher voltage circuits. The voltage limit on V+ will be determined by the V_{DSS} rating of the devices.

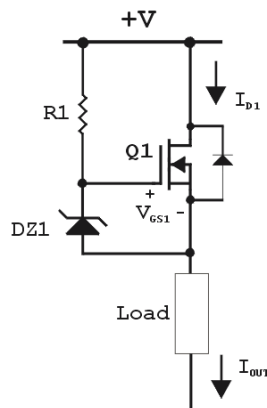


Figure 4: An N-Channel Depletion-mode MOSFET (Q1) as a current source [1]

Figure 5 shows a current source example with a voltage reference IC and a Depletion-mode MOSFET (Q1), which compensates the supply voltage fluctuations. The current source provides a total current to the load comprising the set current through the resistor (R_s) and the IC quiescent current (I_Q). This circuit provides precision current and ultra-high output impedance.

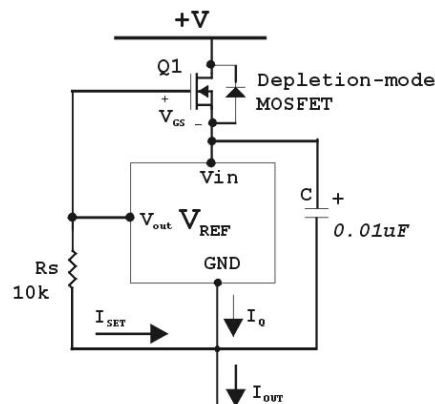


Figure 5: An N-Channel Depletion-mode MOSFET with a voltage reference to provide a precise current source [1]

Figure 6 shows an NMOS inverter circuit that uses a depletion-mode MOSFET as a load. The depletion-mode MOSFET (Q1) acts as a load for the enhancement-mode MOSFET (Q2), which acts as a switch.

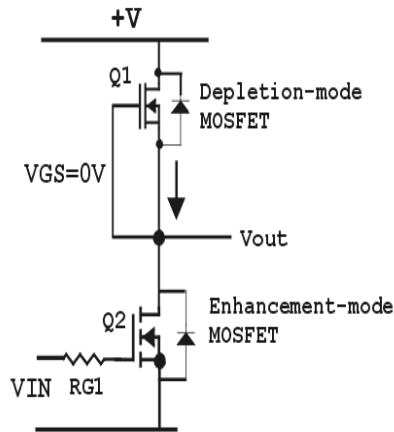


Figure 6: A NMOS Inverter with Depletion-mode device is used as a load [2]

Many applications in industrial and consumer electronics require off-line switch-mode power supplies that operate from wide voltage variations of 110 VAC to 260 VAC. Figure 7 shows such a power supply that uses a depletion-mode MOSFET (Q1) to kick-start the off-line operation by providing initial power to the IC (U1) through the source of Q1.

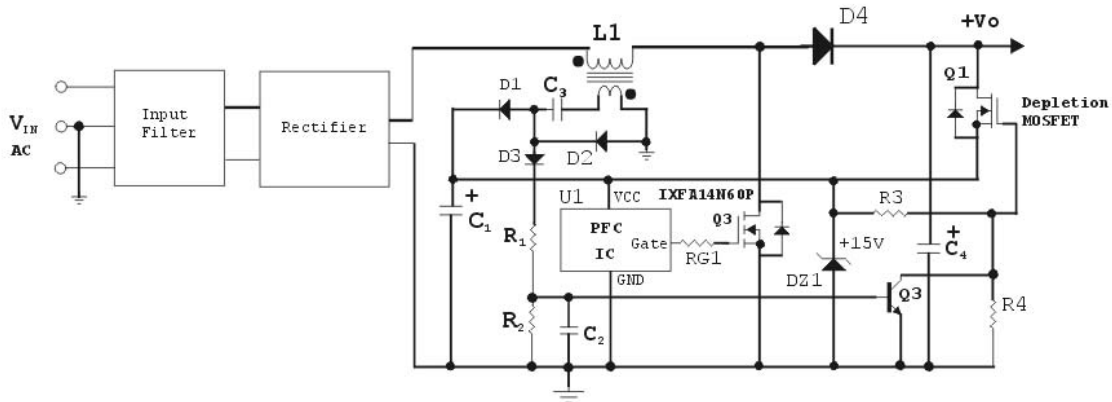


Figure 7: Power Supply start-up circuit using Depletion-mode MOSFET

Q1 provides initial power from the output (V_o). R3 and R4 setup a working point to obtain the minimum required current from Q1. The Zener diode DZ1 limits the voltage across the IC (U1) to +15V. After the start-up, the secondary winding of boost inductor L1 generates the supply voltage for the IC through D1, D2 and C3 and enough current through D3 and R1 for the base of Q3 that turns-on and clamps the gate of Q1 to ground.

Depletion-mode MOSFET can be used to design an off-line LED array driver circuit as shown in Figure 8. The light output from the LED array is proportional to the current through it. The LED arrays has low forward voltage of 3 to 4V and require constant-current drive for optimal operation. They are typically low power devices (1W to 3W) with drive currents in the range of 350mA to 700mA.

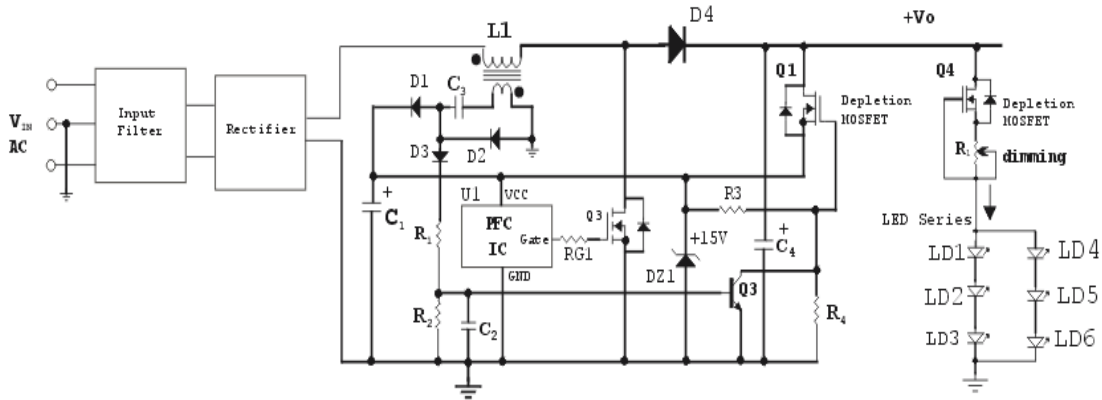


Figure 8: An off-line LED lighting application using Depletion-mode MOSFET

Applications such as high voltage sweeping and automatic test equipment require high voltage ramp with a linear relationship between output voltage and time. Figure 9 utilizes one Depletion-mode MOSFET to design a voltage-ramp generator circuit.

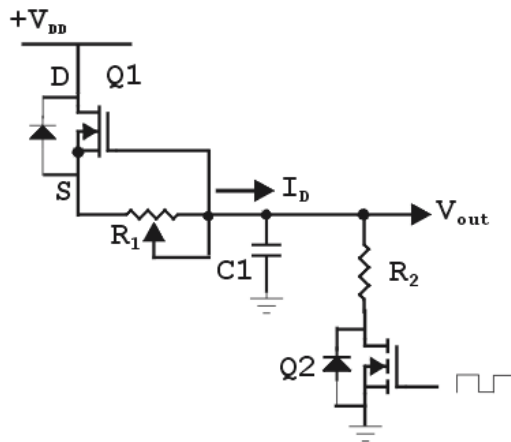


Figure 9: A high voltage ramp generator using one Depletion-Mode (Q1) and one Enhancement-Mode (Q2) N-Channel MOSFETs [2]

Q1 is configured as a constant current source charging a capacitor, C1, and R1 provides negative feedback to regulate and set the desired current value. The constant current source charges the capacitor C1 and generates a voltage ramp, V_{OUT} across the capacitor. The Q2 can be turned on with TTL or CMOS control signal to reset the ramp voltage, by discharging the capacitor to ground through R2. The resistor R2 is used to limit the discharge current for Q2 to operate within its SOA rating.

Initially Q1 is ON because it's turned-on when its gate-to-source voltage, $V_{GS} = 0V$. Any voltage applied on $+V_{DD}$ will create a current that will follow the MOSFET Q1 and charge the capacitor, C1. As the voltage across C1 increases, the output voltage, V_{OUT} , will start to increase until it reaches its regulated voltage of 5.0V.

Q1 acts as a source-follower with its gate (G) is connected to a fixed 5.0V output. The voltage on S will follow the voltage on G, minus V_{GS} . This results, $V_S = V_{OUT} - V_{GS}$, where V_{GS} is the voltage required to supply the input current.

Assume the ramp voltage, $\frac{dV}{dt} = 0.1V / \mu S$

The capacitor C1 value should be small enough to reduce charging and discharging a larger amount of energy and large enough so that output loads and stray capacitances will not introduces significant error. C1 is chosen to be 10.0 nF.

The charging current is defined as $I = C_1 \cdot \frac{dV}{dt}$ (3)

$$I = 1.0nF \cdot 0.1V / \mu S = 100\mu A$$

R1 value for 100 μA current source can be determined using the equation (2):

$$R_1 = \frac{V_{GS(off)}}{I_D} \left(\sqrt{\frac{I_D}{I_{DSS}}} - 1 \right)$$

Where,

$V_{GS(off)}$ = Pinch-off voltage = -4.0V (Choosing a value between minimum -2.5V to maximum -5.0V)

I_{DSS} = Saturation current = 200 mA

$$I_D = 100\mu A$$

$$R_1 = \frac{-4.0}{100\mu A} \left(\sqrt{\frac{100\mu A}{200mA}} - 1 \right) = \frac{-4.0}{100\mu A} (0.0224 - 1) = \frac{3.9106 \times 1000000}{100} = 39.1k\Omega$$

Assume the switching frequency for Q2 is $f_{sw} = 250$ Hz and the discharge time is

$$t_{Dis-ch} = 100\mu s .$$

Power loss in the output capacitor, C1:

$$P = \frac{1}{2} \cdot C1 \cdot V^2 \cdot f_{sw} \quad (4)$$

Using equation (7),

$$P = \frac{1}{2} \cdot 10nF \cdot 400^2 \cdot 250Hz = 800\mu J \cdot 250Hz = 200mJ / S = 200mW$$

Discharging time, $t_{Dis-ch} = 4 \cdot R2C1$ (5)

Using equation (8),

$$R_2 = \frac{100\mu s}{4 \cdot 10nF} = 10k\Omega$$

Many applications require linear voltage regulator that operates from high input voltage and comes from a wide voltage variations of 120 VAC to 240 VAC that corresponds to a maximum peak voltage of +/- 340V. Applications like CMOS ICs and small analog circuits require 5 to 15V DC power supply and need protection from very fast, high voltage transients and low quiescent current from linear regulator. Figure 10 shows a high voltage off-line linear voltage regulator using Depletion-mode MOSFET that can meet the above requirement of low transient voltage and low quiescent current.

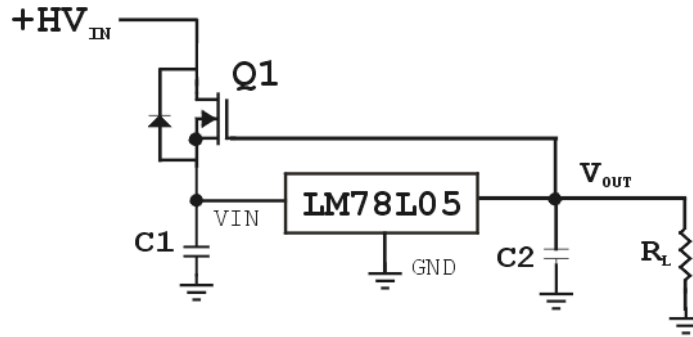


Figure 10: High Voltage Off-line Linear Voltage Regulator [2]

High voltage transients are generated in telecommunication circuits because of lightning and spurious radiations and in automotive and avionics circuits because of inductive loads. The low quiescent current is required to minimize power dissipation in these linear regulators.

HVIN Calculation:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 \quad \text{Solving for } V_{GS} = V_{GS(off)} \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

Where,

$$V_{GS} = V_{OUT} - V_{IN} \quad \text{and} \quad I_{DSS} = \int (V_{GS(th)})$$

$$HVIN = V_{OUT} - V_{GS(off)} \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right) \quad (6)$$

Using equation (1),

$$HVIN = 5.0 + 4 \cdot \left(1 - \sqrt{\frac{10mA}{100mA}} \right) = 5.0 + 4 \cdot (1 - 0.3162) = 7.7352V$$

Current-Monitor Circuit:

A simple current monitor circuit using an op-amp and a Depletion-Mode MOSFET is shown in Figure 11. R₁ monitors the current to the load and the MOSFET, Q1, provides an output voltage proportional to the current being monitored.

$$V_{OUT} = I_{LOAD} \cdot \left(\frac{R_s \cdot R_2}{R_1} \right) \quad (7)$$

The resistance value of R₁ should be a quality of 0.1% wire wound type with appropriate wattage rating.

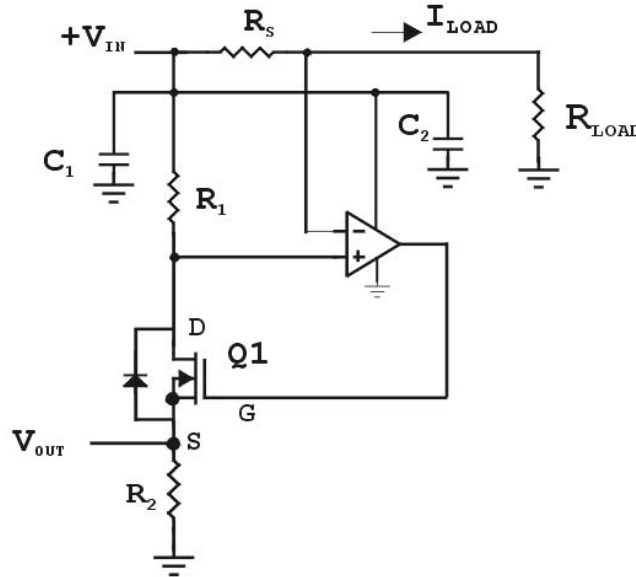


Figure 11: Current monitor using Depletion-Mode MOSFET and a single-supply op-amp.

For example,

$R_s = 0.1 \Omega$, 0.1%, $R_1 = 100 \Omega$, $R_2 = 1 \text{ k}\Omega$

Using equation (7)

$$\frac{V_{OUT}}{I_{LOAD}} = \frac{R_s \cdot R_2}{R_1} = \frac{0.1 \cdot 1000}{100} = 1 \text{ V/A}$$

References:

[1] An introduction to depletion-mode MOSFETs, By Linden Harrison, Advanced Linear Devices, Inc

[2] LND1 Series, Application Note, AN-D16, Supertex Inc.